

## Parallel Circuits

### Parallel Circuits

- In a parallel circuit there are multiple paths for the current.
- Total resistance for resistors in parallel is equal to the inverse of the sum of the inverses of the individual resistors.

$$R_T = \left( \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots} \right)$$

or

$$R_T = \frac{1}{R_1^{-1} + R_2^{-1} + R_3^{-1} \dots}$$

or

$$R_T = (R_1^{-1} + R_2^{-1} + R_3^{-1} \dots)^{-1}$$

### Kirchoff's Rules

#### Important Stuff for Circuits

- Loop rule (KVL):
  - The sum of the voltage around a closed loop is zero.
- Junction rule (KCL):
  - The sum of the current entering a junction is equal to the sum of the current leaving the junction

### Sample Circuit

Known:  $V_{AB} = 12 \text{ V}$

- Draw **current** and **voltage** arrows
- Given  $V_{AB} = 12 \text{ V}$
- Determine the  $R_T$ 
  - $R_T = (3^{-1} + 12^{-1})^{-1} = 2.4 \Omega$
- Determine  $I_1$  ( $V_{AB} = I_1 R_T$ )
  - $12 \text{ V} = I_1 (2.4 \Omega) = 5 \text{ A}$
- Use the loop rule (KVL) to determine the voltage at each resistor
- Use  $V = I R$  at each resistor to determine  $I_2$  and  $I_3$
- Junction rule (KCL)
  - For this circuit
  - $I_1 = I_2 + I_3$
  - $5 \text{ A} = 4 \text{ A} + 1 \text{ A}$  ✓

$I_1 = 5 \text{ A}$   
 $R_T = 2.4 \Omega$

### Practice

$I_1 = 4 \text{ A}$   
 $I_2 = 3 \text{ A}$   
 $I_3 = 1 \text{ A}$   
 $R_T = 2.25 \Omega$   
 $V_{AB} = 9 \text{ V}$

### Practice

$I_1 = 6 \text{ A}$   
 $I_2 = 4.5 \text{ A}$   
 $I_3 = 1.5 \text{ A}$   
 $R_T = 15 \Omega$   
 $V_{AB} = 90 \text{ V}$   
 $V_{AC} = 60 \text{ V}$   
 $V_{CB} = 30 \text{ V}$