

CALCULATING COMBINATION CIRCUITS

- A "COMBINATION CIRCUIT" is (as you may have already guessed) a circuit that is a blend of series paths and parallel paths.
- Most circuits are of this variety.
- Don't be afraid to tackle these circuits as far as the math goes.
- You merely have to break each part of the circuit down into either a series circuit or parallel circuit.



